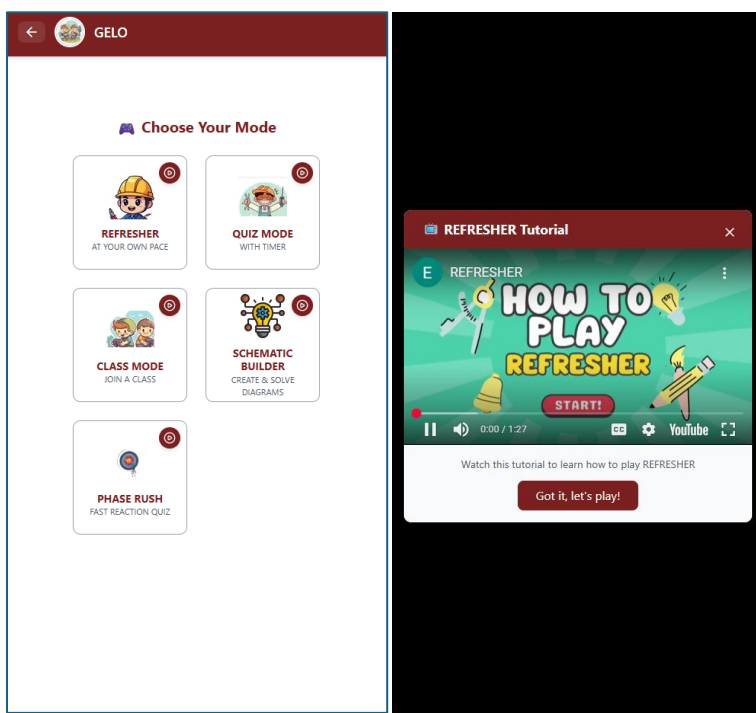



EIM USER MANUAL FOR GAME MODES:




Student can easily view the video tutorial by clicking the play button in the right side of each game mode

REFRESHER:

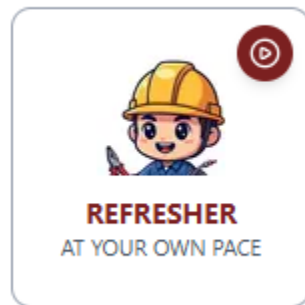
1. Choose **REFRESHER** to start the game




2. Choose the level you wish to play

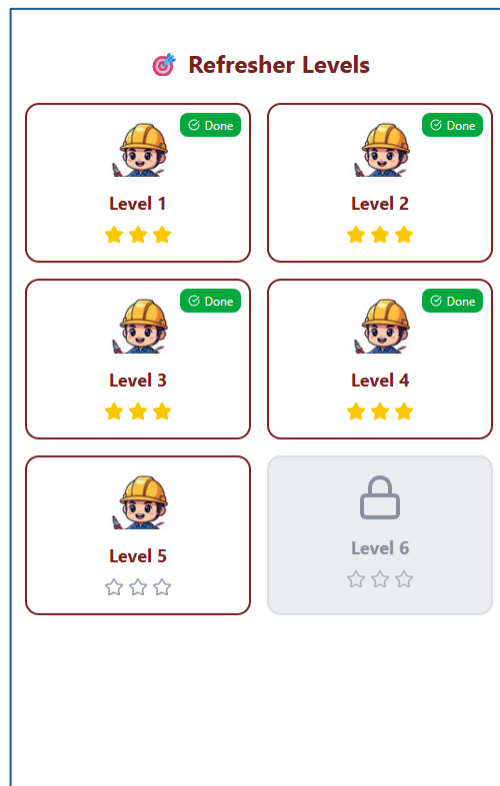

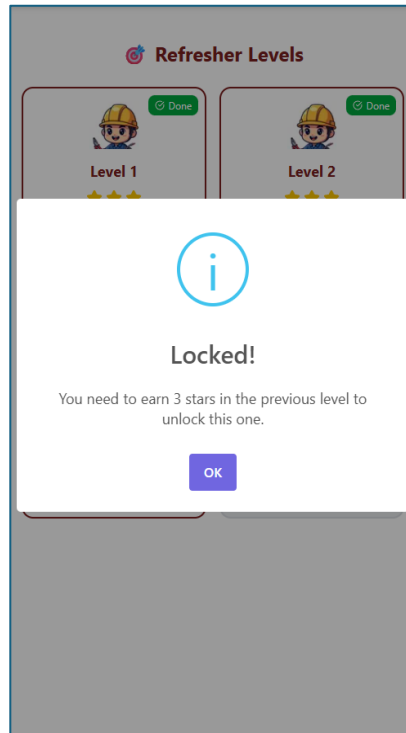3. To unlock the next level, complete the previous level perfectly



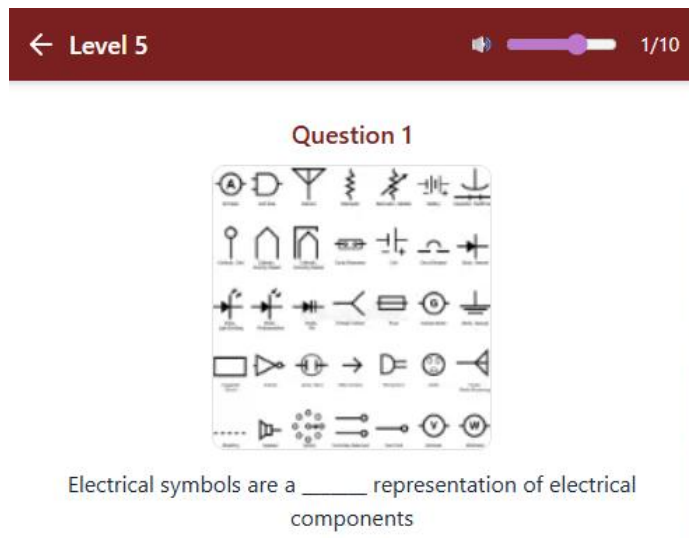
4. Adjust the Volume slider, with your preference volume of the sounds




5. If the answer is correct, it will turn green. Choose NEXT to proceed in next question

Question 1



Electrical symbols are a _____ representation of electrical components

A. Numerical

B. Graphical 

C. Physical

D. Mechanical

Next


6. If the answer is wrong, it will turn to red and it will show you the correct answer indicated with green.

Question 2

Electrical symbols are also called _____

A. Circuit codes



B. Mechanical notations

C. Electrical tags 

D. Schematic symbols

Next

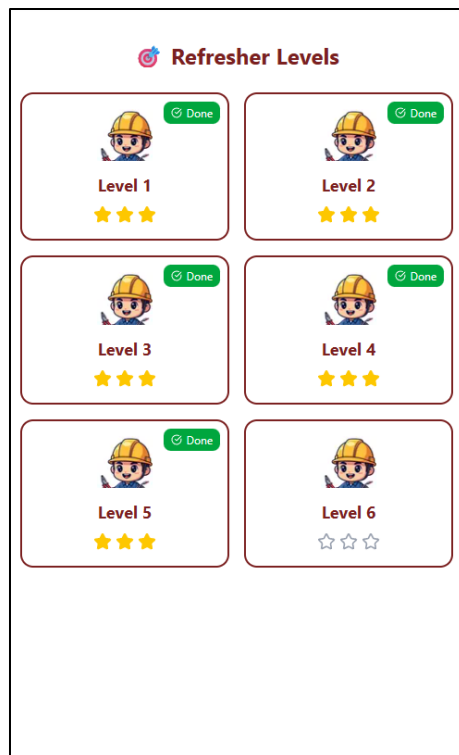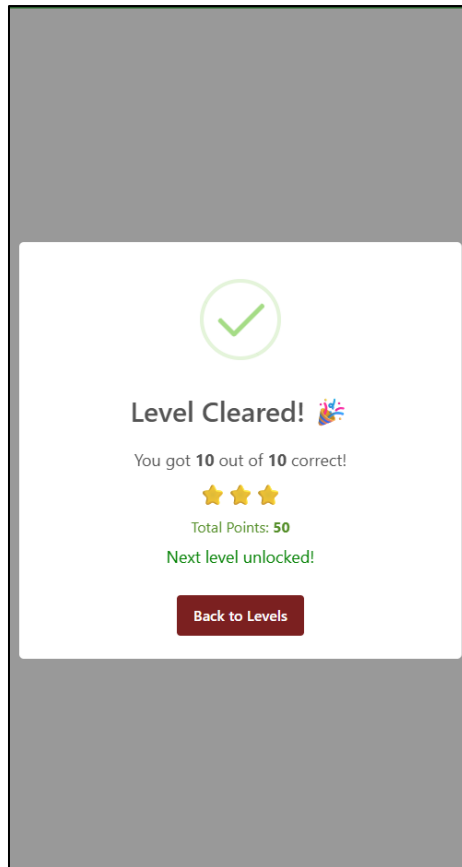7. Complete the game perfectly to unlock the next level




QUIZ MODE:



1. Choose **QUIZ MODE** to begin



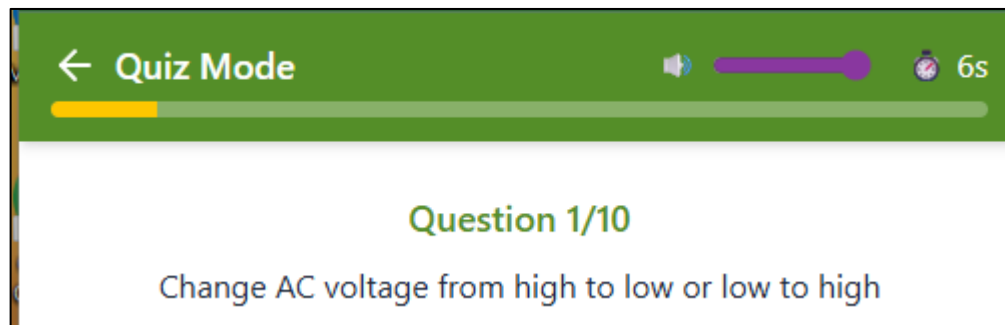2. Adjust the volume slider as needed. The time in the right side corner indicates the timer per question and the progress bar showing yellow is the duration of the game.



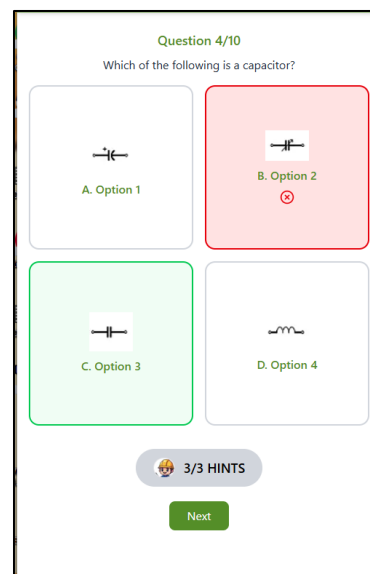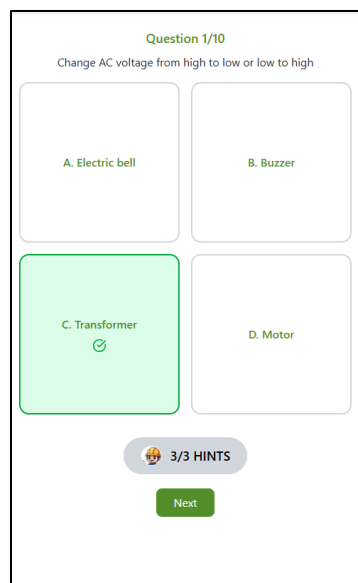
3. When choosing an option, green indicates the correct answer while the red is the wrong answer



4. To filter out the best two options in the given question, use HINT

Question 1/10



Controlled Voltage Source

A. Generates resistance as a function of voltage

B. Generates voltage as a function of voltage


C. Generates capacity as a function of voltage

D. Generates current as a function of voltage


3/3 HINTS

Question 2/10

Which of the following is symbols is a connected wires?



A. Option 1



B. Option 2


2/3 HINTS

5. Once the duration of the game ends or the player answer all of the questions, the game will end immediately and show the result

← Quiz Mode 8s

Question 10/10

Symbols used in schematic diagrams are standardized to ensure



Challenge Complete! 🎉

You got 7 / 10 correct!

Time used: 42s / 60s

Total Points: **210** / 1000

Back to Menu

2/3 HINTS


Finish

SCHEMATIC BUILDER:


1. Choose **SCHEMATIC BUILDER** to begin



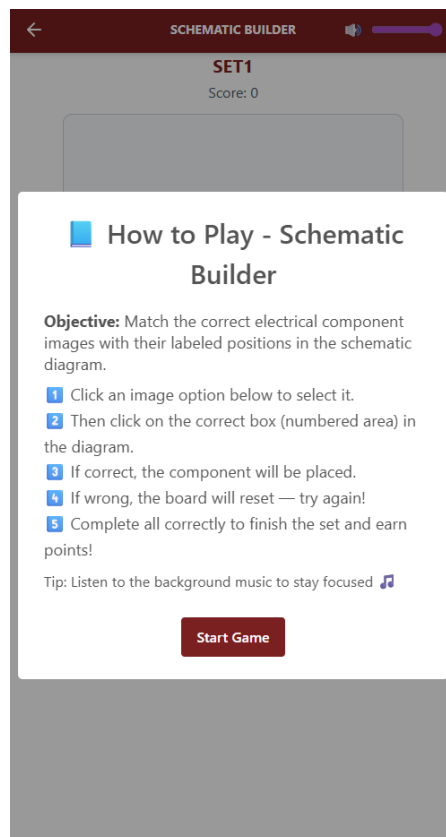
2. Follow the instructions provided to play the game



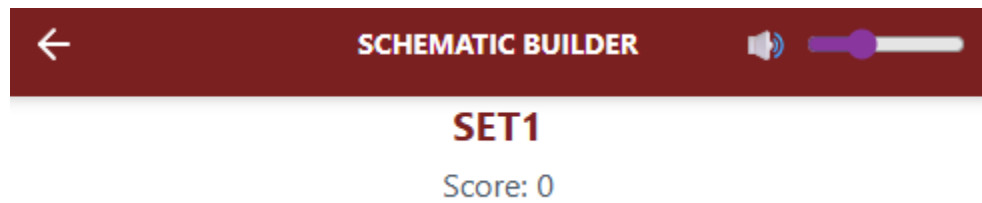
3. Adjust the volume slider for the control of volume



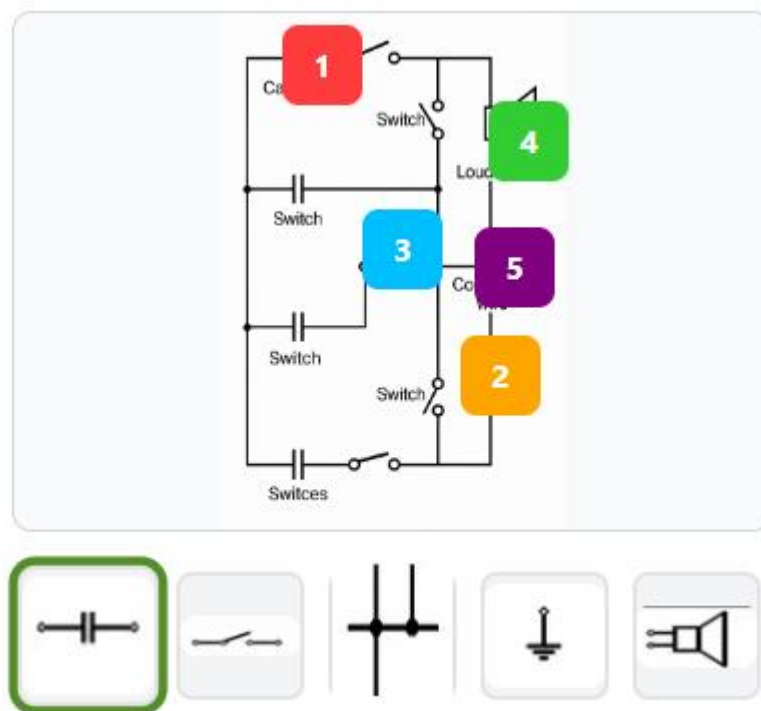
4. Choose the component given in the options, the green indicator indicates that this is the option chosen



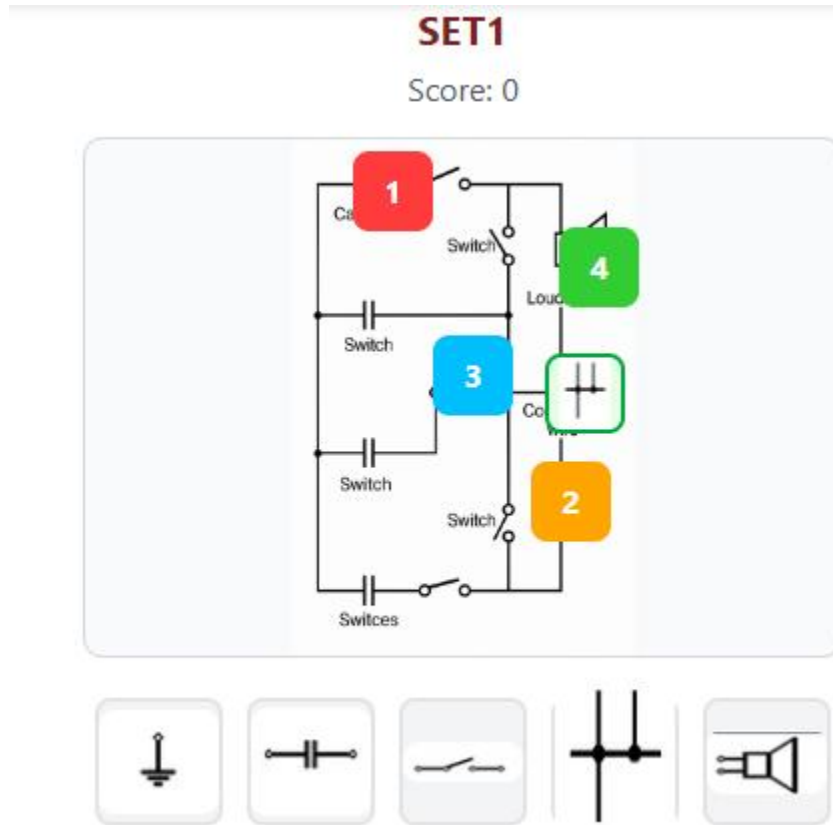
5. Put the selected component to the correct slot, if correct it will show green indicator and the options will not shuffle



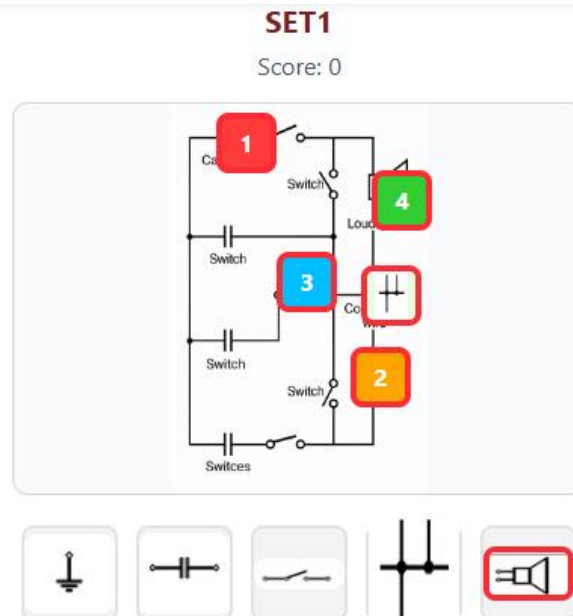6. Putting the wrong component to the slot will indicate a color red indicator and will make the options shuffle there positions




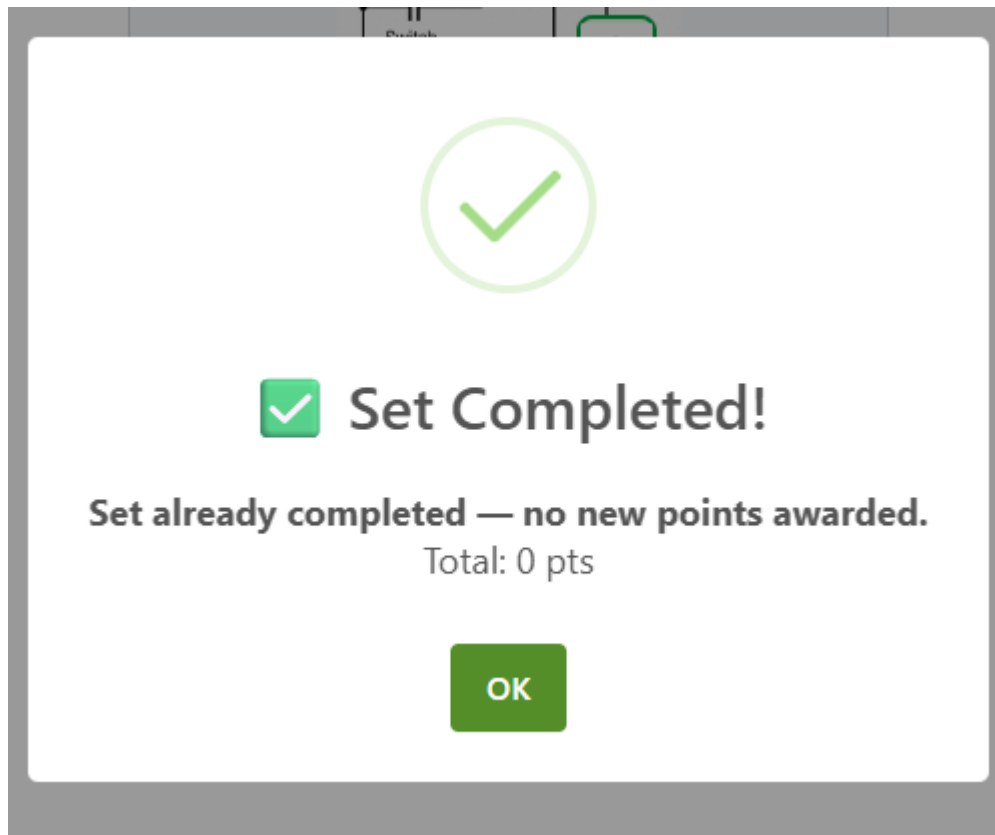7. If the set is already completed before, it will not provide points anymore otherwise it will show the result with designated points



PHASE RUSH:


1. Choose the **PHASE RUSH** to begin

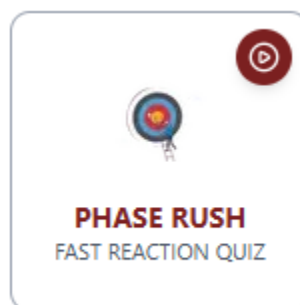



2. Adjust the volume of the game using the volume slider



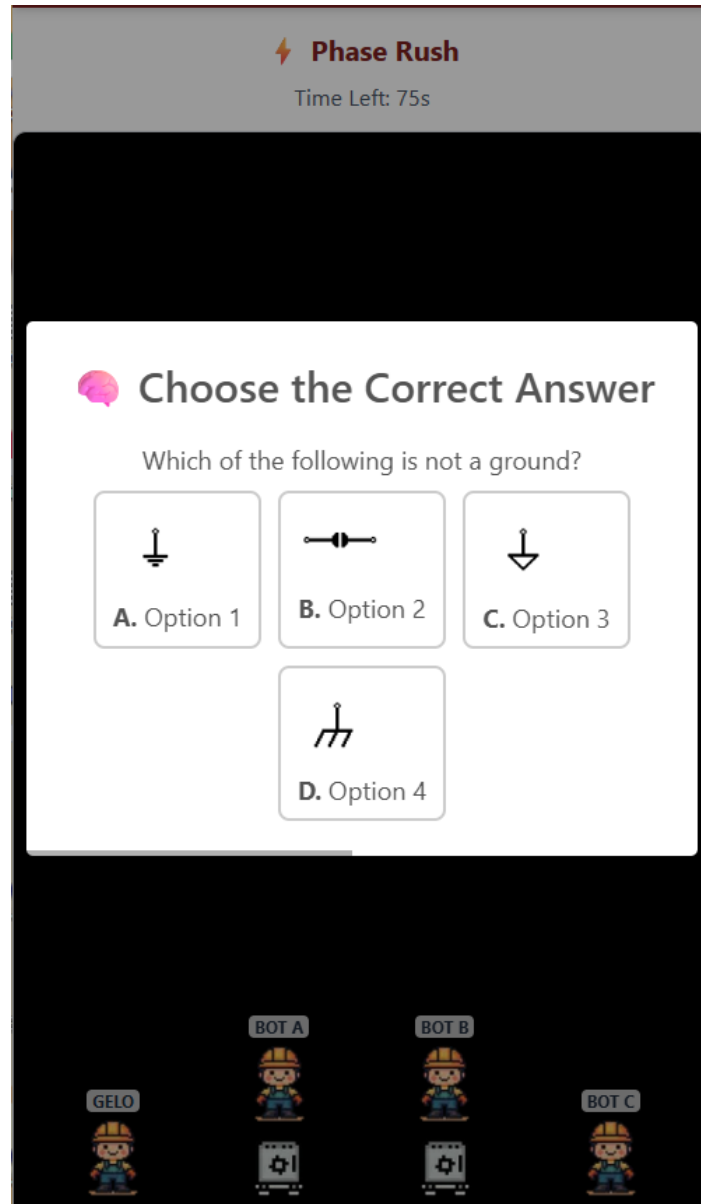
3. Choose the correct answer every time the question pop ups.



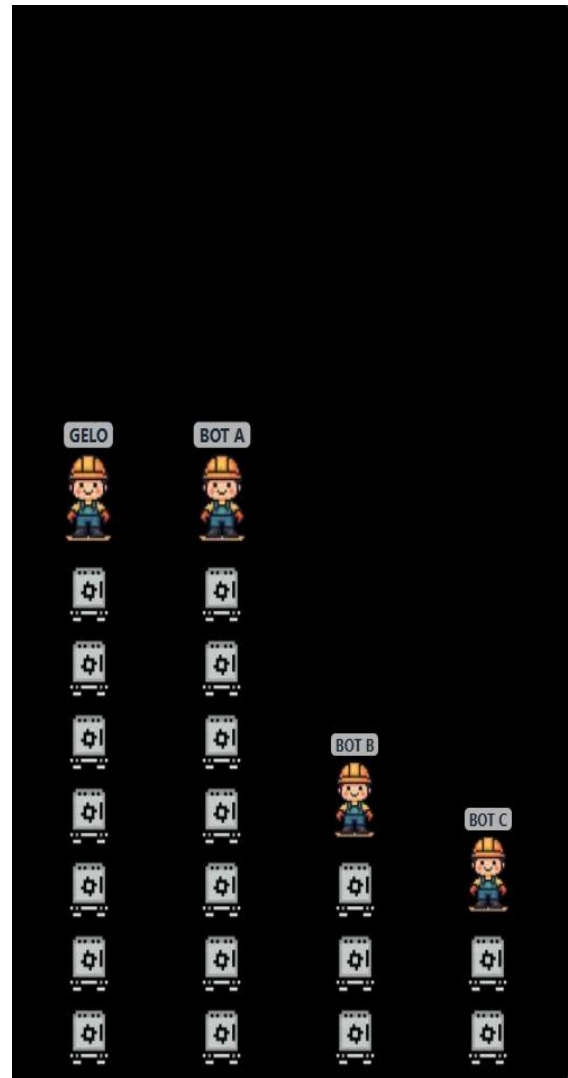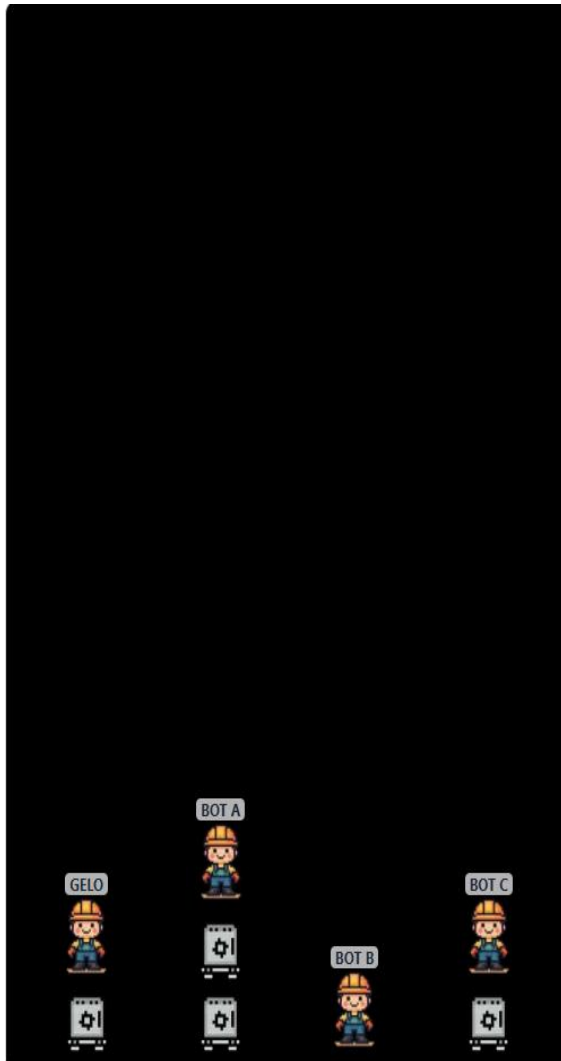4. For every correct answer, the character will go up, and for every wrong answer the character will go down











5. Once the timer ends, it will show the result of the ranking



Game Over!

Final Rankings


Correct: 1 | Wrong: 1 | Total: 2
Accuracy: 50.0%

	BOT A	
3	3 ✓ 0 ✗ (100.0%)	
	BOT C	
2	2 ✓ 1 ✗ (66.7%)	
	GELO	
1	1 ✓ 1 ✗ (50.0%)	
	BOT B	
1	1 ✓ 2 ✗ (33.3%)	



[Return to Menu](#)

CLASS MODE:


1. Choose **CLASS MODE** to begin

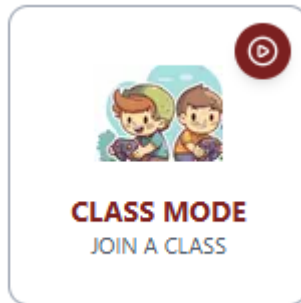


2. Put the game code that will be provided by your teacher

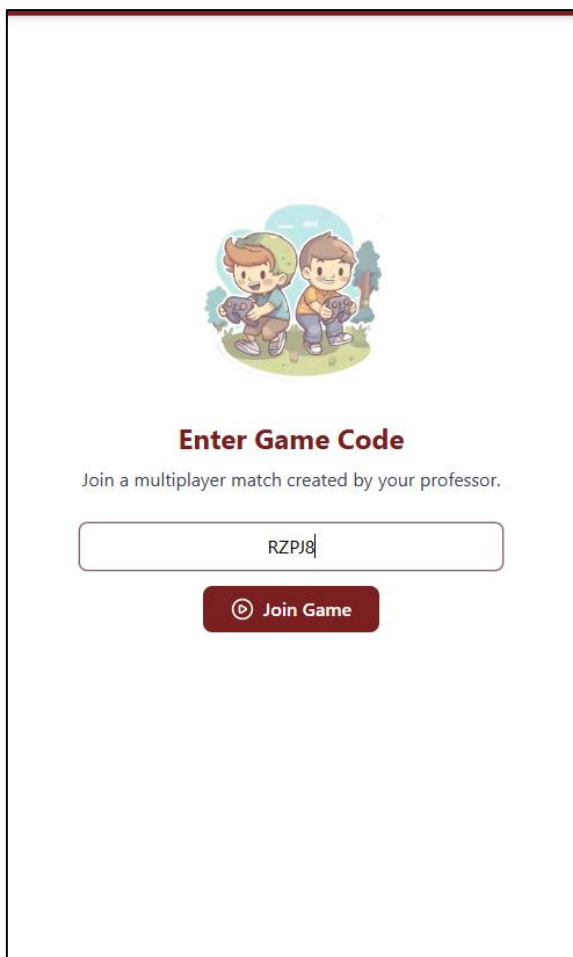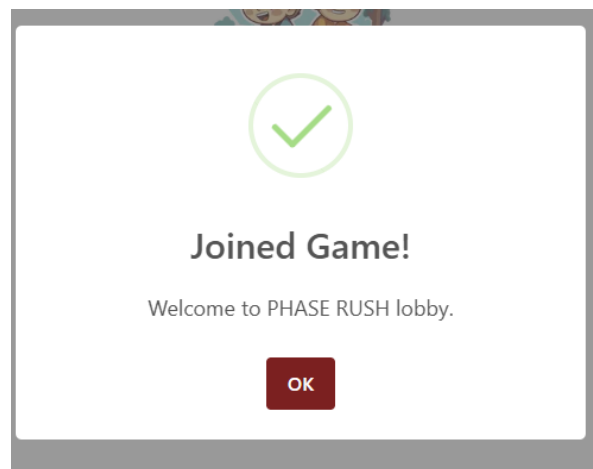A screen with a white background. At the top center is an illustration of two cartoon boys holding video controllers. Below the illustration, the text "Enter Game Code" is written in bold red capital letters. Underneath that, in smaller black text, it says "Join a multiplayer match created by your professor." Below this text is a white rectangular input field with a thin border. Inside the field, the text "RZPJ8" is entered. Below the input field is a red button with rounded corners. On the left of the button is a small red circular icon with a white play button symbol, followed by the text "Join Game" in white.

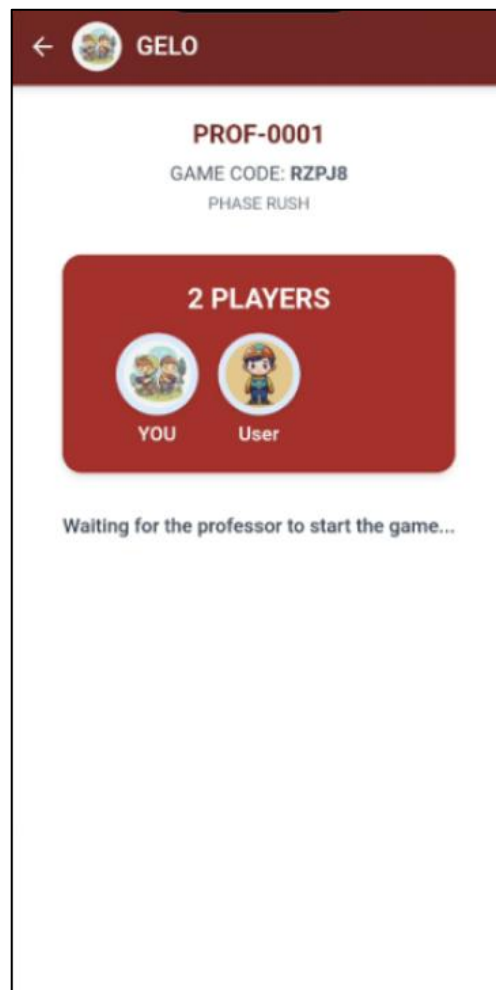3. Once successful, wait for the teacher to start the game



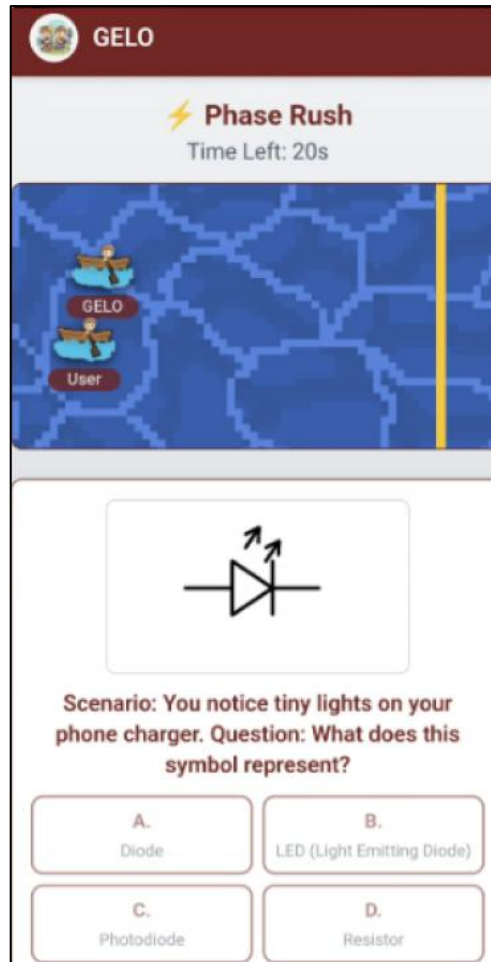4. For every correct answer, your character will move forward and for every wrong answer your character will move backward. Finish the game until the duration of the game ends



5. Once the game is completed, it will show the ranking for that game

